

Assignment Project Exam Help

Lecture 10

<https://tutorcs.com>


WeChat: cstutorcs

Recap : Boolean Circuit

V, \wedge, \neg , in-degree ≤ 2 .
XOR : XOR (addition mod 2) . $1+1=0$
 $1+0=1$
 $0+0=0$

Assignment Project Exam Help

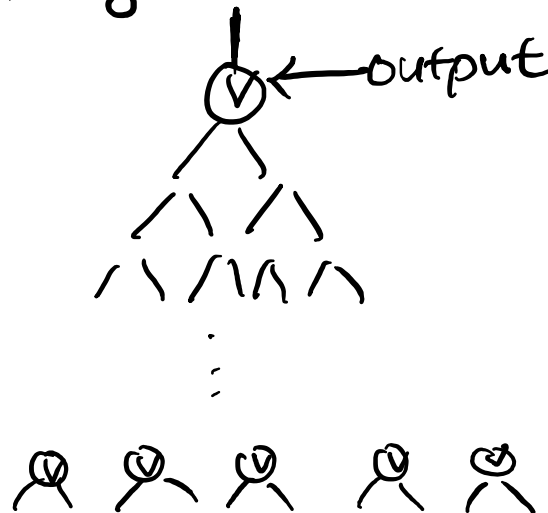ex Computing OR of n -bits <https://tutorcs.com>



WeChat: cstutorcs

All functions can be computed by circuit

boolean

exponentially many gates.

proof via induction

$$S(1) = O(1)$$

base case ✓

Assignment Project Exam Help

$$S(k+1)$$

induction

input bits $\leq k$

can be computed

$$\text{via ckt. } \leq 2 \cdot S(k) + O(1)$$

<https://tutorcs.com>

$$S(n) ? \Rightarrow S(1) \leq 2^n$$

$$f: \{0,1\}^{k+1} \rightarrow \{0,1\}$$

$$\rightarrow \{0,1\}$$

WeChat: cstutorcs

each G has corresponding Boolean ckt.


$$f|_{x_1=1}: \{0,1\}^k \rightarrow \{0,1\} \xrightarrow{f} \{0,1\}$$



C_1

$$f|_{x_1=0}: \{0,1\}^k \rightarrow \{0,1\}^{k+1}$$

C_0

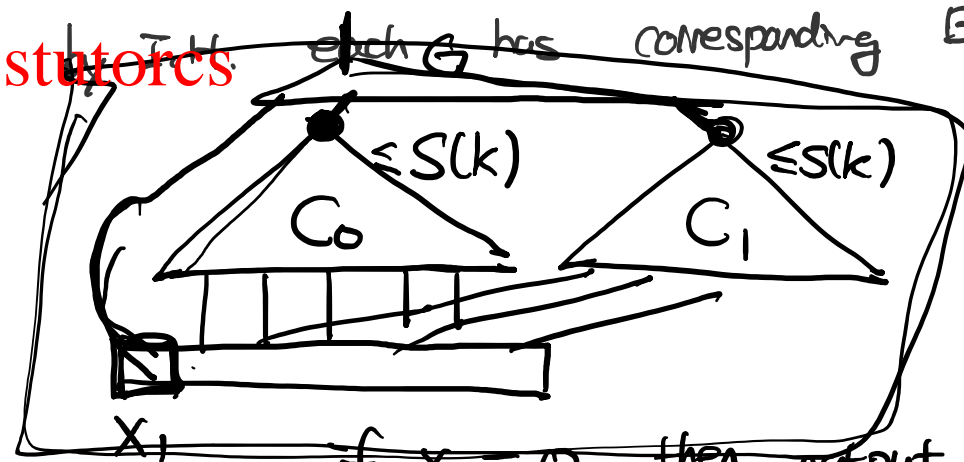

compute f .

$$\Rightarrow \text{all } f: \{0,1\}^{k+1} \rightarrow \{0,1\}$$

has corresponding Boolean ckt.


if $x_1 = 0$, then output C_0

$x_1 = 1$,

"

C_1

Exercise) control bit

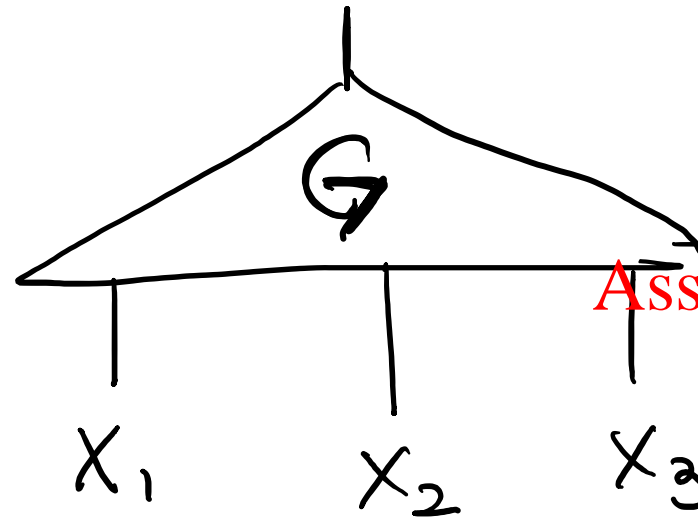

if $x_1 = 0$, output x_2

$x_1 = 1$, output x_3

Assignment Project Exam Help this is double with $O(1)$ -gates.

<https://tutorcs.com>

WeChat: cstutorcs

So for circuit this is ill-posed problem

For every $L \subseteq \{0,1\}^*$, $\exists \{C_n\}_{n \in \mathbb{N}}$ which decides L .

$$\chi_L(x) = \begin{cases} 1 & \text{if } x \in L \\ 0 & \text{if } x \notin L \end{cases}$$

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

Why circuit is interesting to study then?

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

Two unrealistic strength that we gave

- ~~Exponential # of gates~~

poly # of gates

whether or not ~~to~~ has seed family of cks.

- ~~Non-uniform computation~~

Uniform

then it becomes equiv. to T.M.

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

Instead, suppose we reduce # of gates

- $O(2^n)$ -gates to compute any f

bad and
unrealistic

Assignment Project Exam Help

$\text{poly}(n)$ -gates . to compute any f ?

<https://tutorcs.com>

WeChat: cstutorcs

Shannon's counting argument

With $C \xrightarrow{\text{poly}(n)}$ # of gates, you can compute $2^{\tilde{O}(C)}$ many functions

Total # of functions with n boolean input. 2^{2^n}



Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

$$2^{O(\text{poly}(n))} \lll 2^{2^n}$$

$$2^{2^n}$$

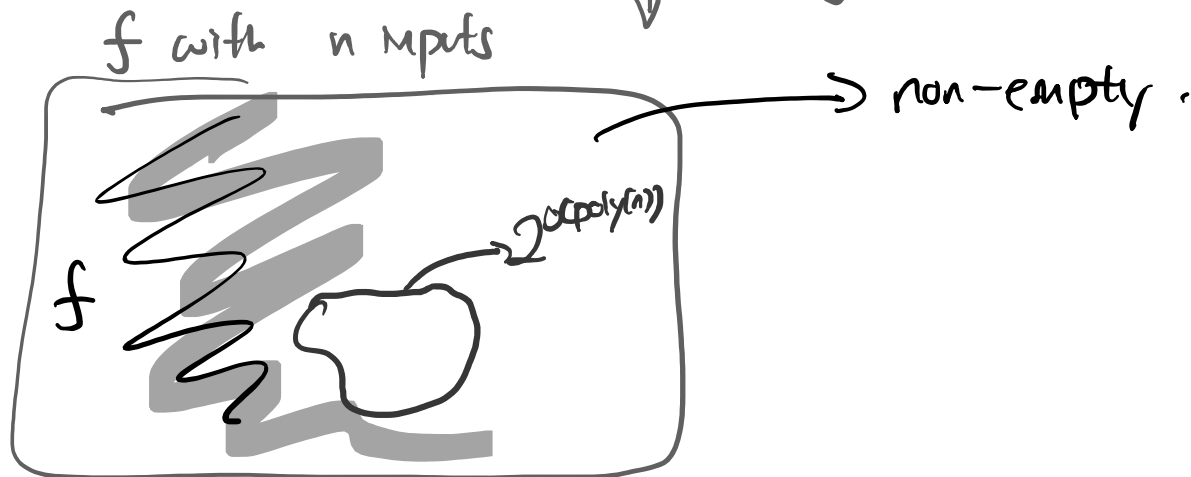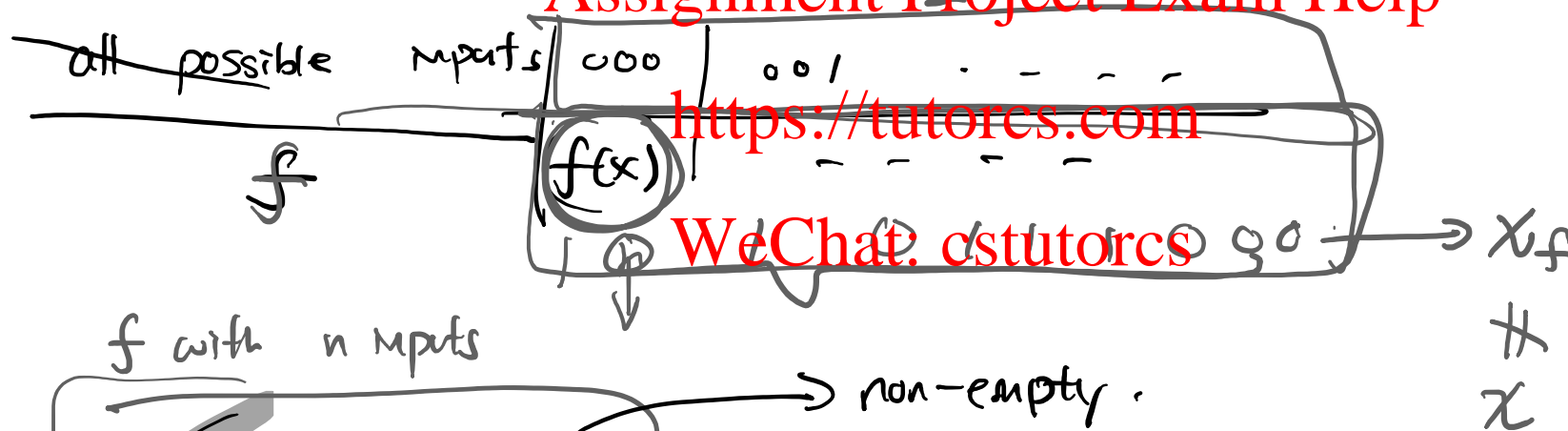


Side Note : Claude Shannon

- Father of Information Theory
- How to transmit message efficiently from A to B? – related to physics
- Need to obtain information before computing on top of it

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

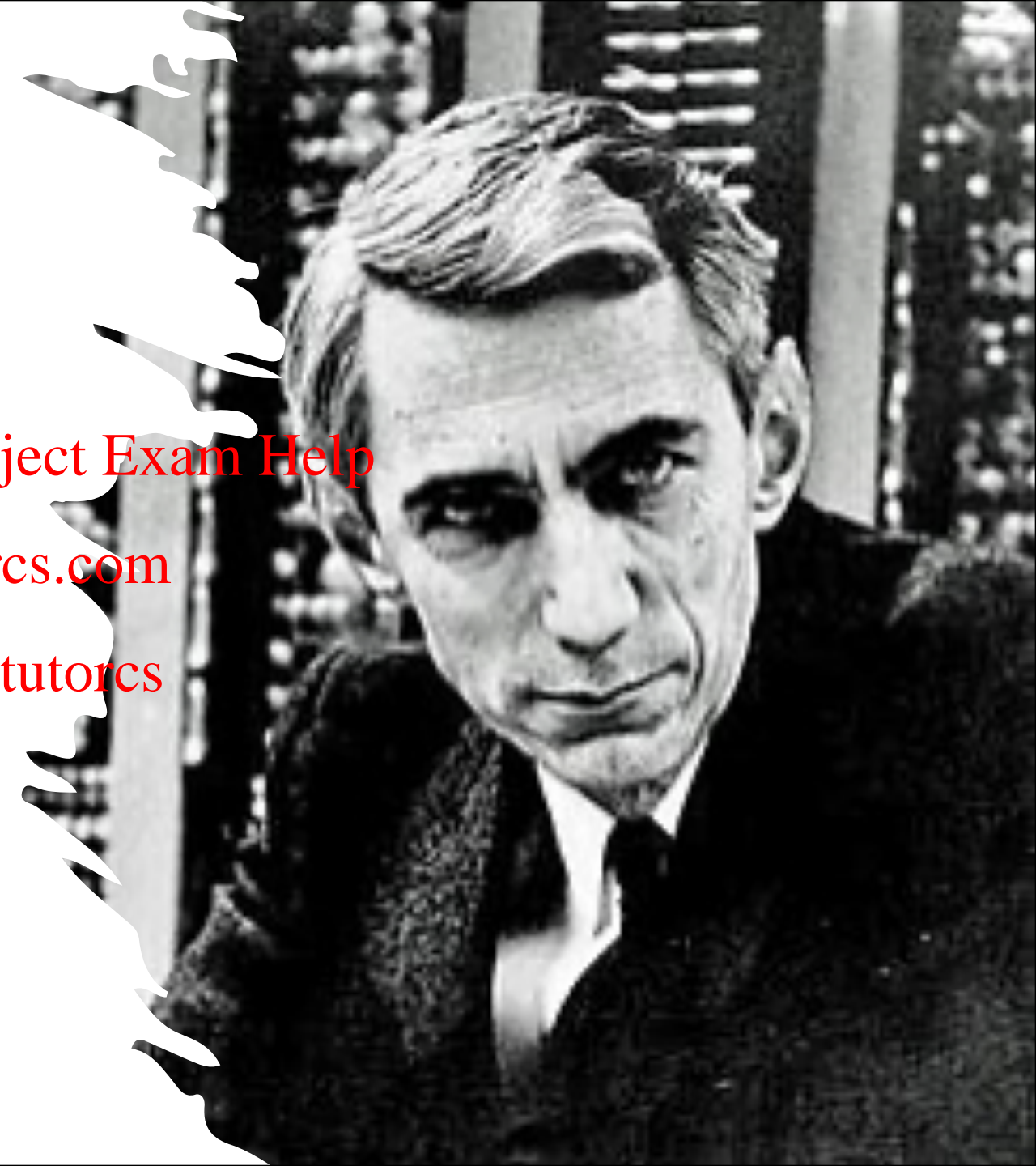

Total # of possible Boolean Functions

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

of possible circuits with K gates

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs


If fewer gates then ... ?

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

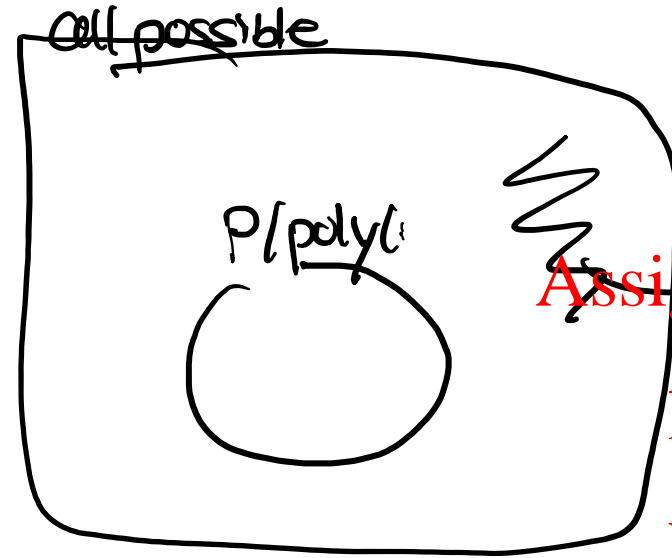Regime of interest : $\text{poly}(n)$ gates : **P/poly**



~~Assignment Project Exam Help~~

<https://tutorcs.com>

WeChat: cstutorcs

Non-uniformity ?

Uniform model of comp.

Uniform Ckts :

Output circuit using TM.

Given $\underbrace{1 \dots 1}_n \exists \text{ T.M must output } \langle C_n \rangle$
ex) OR, AND.


Assignment Project Exam Help

Uniform Ckt \Leftrightarrow T.M.

<https://tutorcs.com>

WeChat: cstutorcs

wordRAM Model

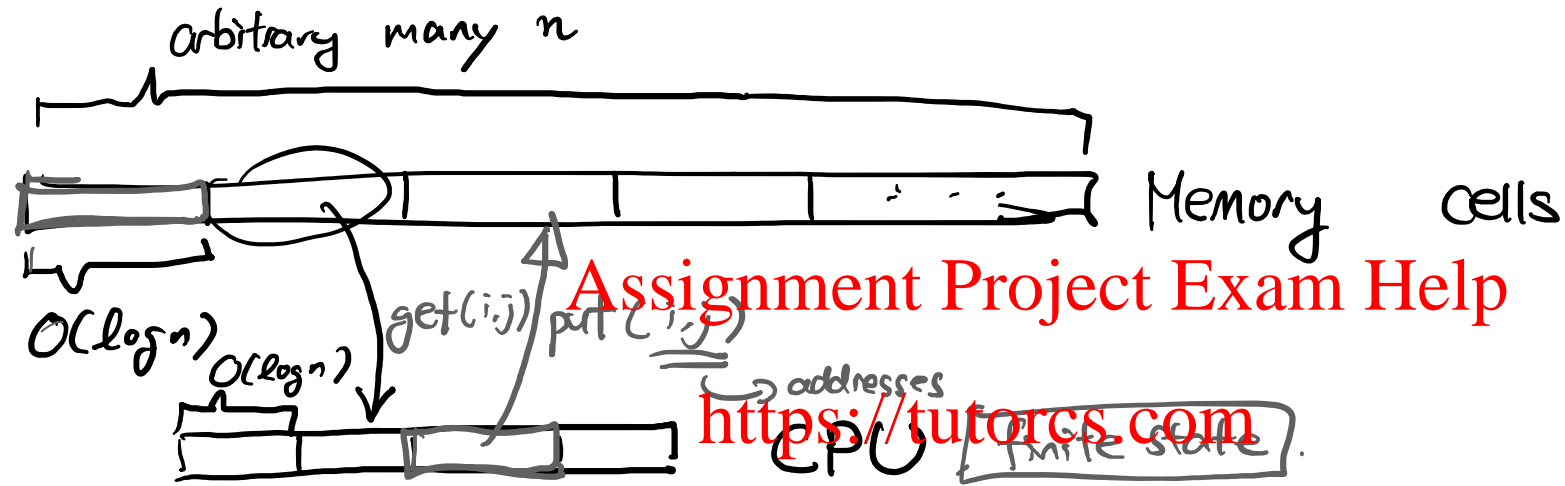

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

• get ; put, basic arithmetics in CPU, (with in CPU),
 $+ \times, -, \div, \&$, shift operations.
 • copy CPU.
 • unit operations.

T.M. \Leftrightarrow wordRAM .